

# Digital Logic Design + Computer Architecture


Sayandeep Saha

Assistant Professor  
Department of Computer  
Science and Engineering  
Indian Institute of Technology  
Bombay



# Sequential Circuits

# General View of a Hardware: Once Again

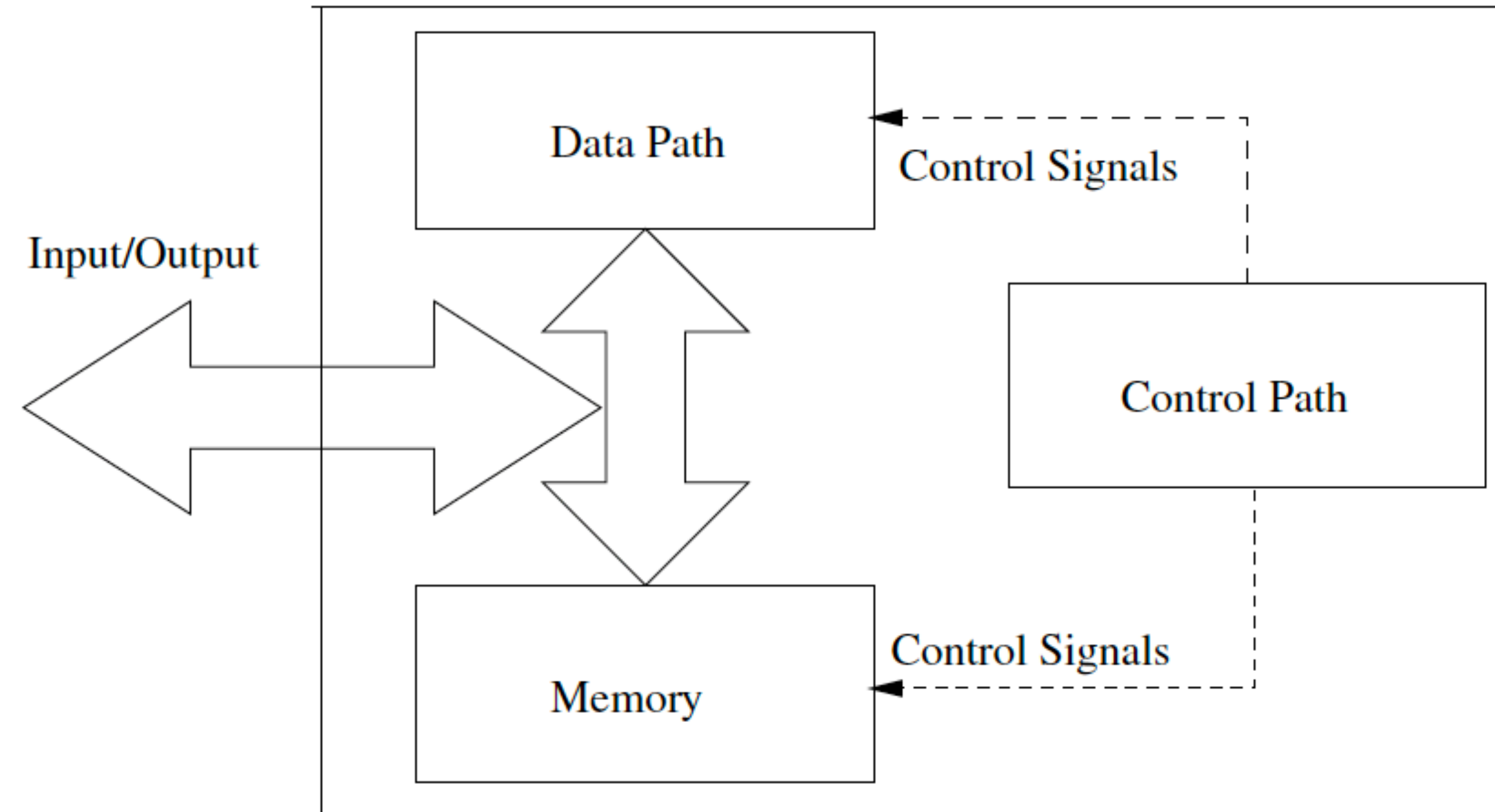

# Binary GCD Algorithm

**Input:** Integers  $u$  and  $v$

**Output:** Greatest Common Divisor of  $u$  and  $v$ :  $z = \gcd(u, v)$

```
1 while ( $u \neq v$ ) do
2   if  $u$  and  $v$  are even then
3      $z = 2\gcd(u/2, v/2)$ 
4   end
5   else if ( $u$  is odd and  $v$  is even) then
6      $z = \gcd(u, v/2)$ 
7   end
8   else if ( $u$  is even and  $v$  is odd) then
9      $z = \gcd(u/2, v)$ 
10  end
11  else
12    if ( $u \geq v$ ) then
13       $z = \gcd((u - v)/2, v)$ 
14    end
15    else
16       $z = \gcd(u, (v - u)/2)$ 
17    end
18  end
19 end
```

# Binary GCD Algorithm: Closer to Hardware

**Input:** Integers  $u$  and  $v$

**Output:** Greatest Common Divisor of  $u$  and  $v$ :  $z = \gcd(u, v)$

```
1 while ( $u \neq v$ ) do
2   if  $u$  and  $v$  are even then
3      $z = 2\gcd(u/2, v/2)$ 
4   end
5   else if ( $u$  is odd and  $v$  is even) then
6      $z = \gcd(u, v/2)$ 
7   end
8   else if ( $u$  is even and  $v$  is odd) then
9      $z = \gcd(u/2, v)$ 
10  end
11  else
12    if ( $u \geq v$ ) then
13       $z = \gcd((u - v)/2, v)$ 
14    end
15    else
16       $z = \gcd(u, (v - u)/2)$ 
17    end
18  end
19 end
```

**Input:** Integers  $u$  and  $v$

**Output:** Greatest Common Divisor of  $u$  and  $v$ :  $z = \gcd(u, v)$

```
1 register  $X_R, Y_R$ ;
2  $X_R = u; Y_R = v; count = 0$ ;
3 while ( $X_R \neq Y_R$ ) do
4   if ( $X_R[0] = 0$  and  $Y_R[0] = 0$ ) then
5      $X_R = \text{right shift}(X_R)$ 
6      $Y_R = \text{right shift}(Y_R)$ 
7      $count = count + 1$ 
8   end
9   else if ( $X_R[0] = 1$  and  $Y_R[0] = 1$ ) then
10     $Y_R = \text{right shift}(Y_R)$ 
11  end
12  else if ( $X_R[0] = 0$  and  $Y_R[0] = 1$ ) then
13     $X_R = \text{right shift}(X_R)$ 
14  end
15  else
16    if ( $X_R \geq Y_R$ ) then
17       $X_R = \text{right shift}(X_R - Y_R)$ 
18    end
19    else
20       $Y_R = \text{right shift}(Y_R - X_R)$ 
21    end
22 end
23 while ( $count > 0$ ) do
24    $X_R = \text{left shift}(X_R)$ 
25    $count = count - 1$ 
26 end
```

# Binary GCD Algorithm: Closer to Hardware

**Input:** Integers  $u$  and  $v$

**Output:** Greatest Common Divisor of  $u$  and  $v$ :  $z = \gcd(u, v)$

```
1 while (u!=v) do
2   if u and v are even then
3     z = 2gcd(u/2, v/2)
4   end
5   else if (u is odd and v is even) then
6     z = gcd(u, v/2)
7   end
8   else if (u is even and v is odd) then
9     z = gcd(u/2, v)
10  end
11  else
12    if (u ≥ v) then
13      z = gcd((u - v)/2, v)
14    end
15    else
16      z = gcd(u, (v - u)/2)
17    end
18  end
19 end
```

How to interpret as hardware?

Keep the  
count of the  
2's getting  
multiplied

**Input:** Integers  $u$  and  $v$

**Output:** Greatest Common Divisor of  $u$  and  $v$ :  $z = \gcd(u, v)$

```
1 register XR, YR;
2 XR = u; YR = v; count = 0;
3 while (XR! = YR) do
4   if (XR[0] = 0 and YR[0] = 0) then
5     XR = right shift(XR)
6     YR = right shift(YR)
7     count = count + 1
8   end
9   else if (XR[0] = 1 and YR[0] = 1) then
10    YR = right shift(YR)
11  end
12  else if (XR[0] = 0 and YR[0] = 1) then
13    XR = right shift(XR)
14  end
15  else
16    if (XR ≥ YR) then
17      XR = right shift(XR - YR)
18    end
19    else
20      YR = right shift(YR - XR)
21    end
22  end
23 while (count > 0) do
24   XR = left shift(XR)
25   count = count - 1
26 end
```

# Constructing the Datapath

**Input:** Integers  $u$  and  $v$

**Output:** Greatest Common Divisor of  $u$  and  $v$ :  $z = \gcd(u, v)$

```
1 register  $X_R, Y_R$ ;  
2  $X_R = u; Y_R = v; count = 0$ ;  
3 while ( $X_R \neq Y_R$ ) do  
4   if ( $X_R[0] = 0$  and  $Y_R[0] = 0$ ) then  
5      $X_R = \text{right shift}(X_R)$   
6      $Y_R = \text{right shift}(Y_R)$   
7      $count = count + 1$   
8   end  
9   else if ( $X_R[0] = 1$  and  $Y_R[0] = 1$ ) then  
10     $Y_R = \text{right shift}(Y_R)$   
11  end  
12  else if ( $X_R[0] = 0$  and  $Y_R[0] = 1$ ) then  
13     $X_R = \text{right shift}(X_R)$   
14  end  
15  else  
16    if ( $X_R \geq Y_R$ ) then  
17       $X_R = \text{right shift}(X_R - Y_R)$   
18    end  
19    else  
20       $Y_R = \text{right shift}(Y_R - X_R)$   
21    end  
22 end  
23 while ( $count > 0$ ) do  
24    $X_R = \text{left shift}(X_R)$   
25    $count = count - 1$   
26 end
```

- **Required hardware components**
  - Two Registers for holding  $u$  and  $v$  (sequential)
- **Datapath elements**
  - Subtractor
  - Complementer
  - Right shifter
  - Left shifter
  - Counter (sequential)
  - Multiplexors — to route the control signals


# Constructing the Controller

```
1 register  $X_R, Y_R$ ;
2  $X_R = u; Y_R = v; count = 0;$                                 /* State 0 */
3 while ( $X_R \neq Y_R$ ) do
4   if ( $X_R[0] = 0$  and  $Y_R[0] = 0$ ) then                       /* State 1 */
5      $X_R = \text{right shift}(X_R)$ 
6      $Y_R = \text{right shift}(Y_R)$ 
7      $count = count + 1$ 
8   end
9   else if ( $X_R[0] = 1$  and  $Y_R[0] = 1$ ) then                 /* State 2 */
10     $Y_R = \text{right shift}(Y_R)$ 
11  end
12  else if ( $X_R[0] = 0$  and  $Y_R[0] = 1$ ) then                 /* State 3 */
13     $X_R = \text{right shift}(X_R)$ 
14  end
15  else                                                         /* State 4 */
16    if ( $X_R \geq Y_R$ ) then
17       $X_R = \text{right shift}(X_R - Y_R)$ 
18    end
19    else
20       $Y_R = \text{right shift}(Y_R - X_R)$ 
21    end
22 end
23 while ( $count > 0$ ) do                                       /* State 5 */
24    $X_R = \text{left shift}(X_R)$ 
25    $count = count - 1$ 
26 end
```

- **Observation**

- Whenever there is an if-else block, we allocate a state
- **Why? Because they dictate the control flow**
- The while loop is handled by the counter
- Give the counter value to the controller and it tells you when to stop
- **Note:** there might be cases when you have no if-else statements, but you have to sequentialize the computation
  - Remember the  $4a+b$  example.
  - Whenever you need to sequentialise, allocate states.

# Constructing the Hardware Diagram

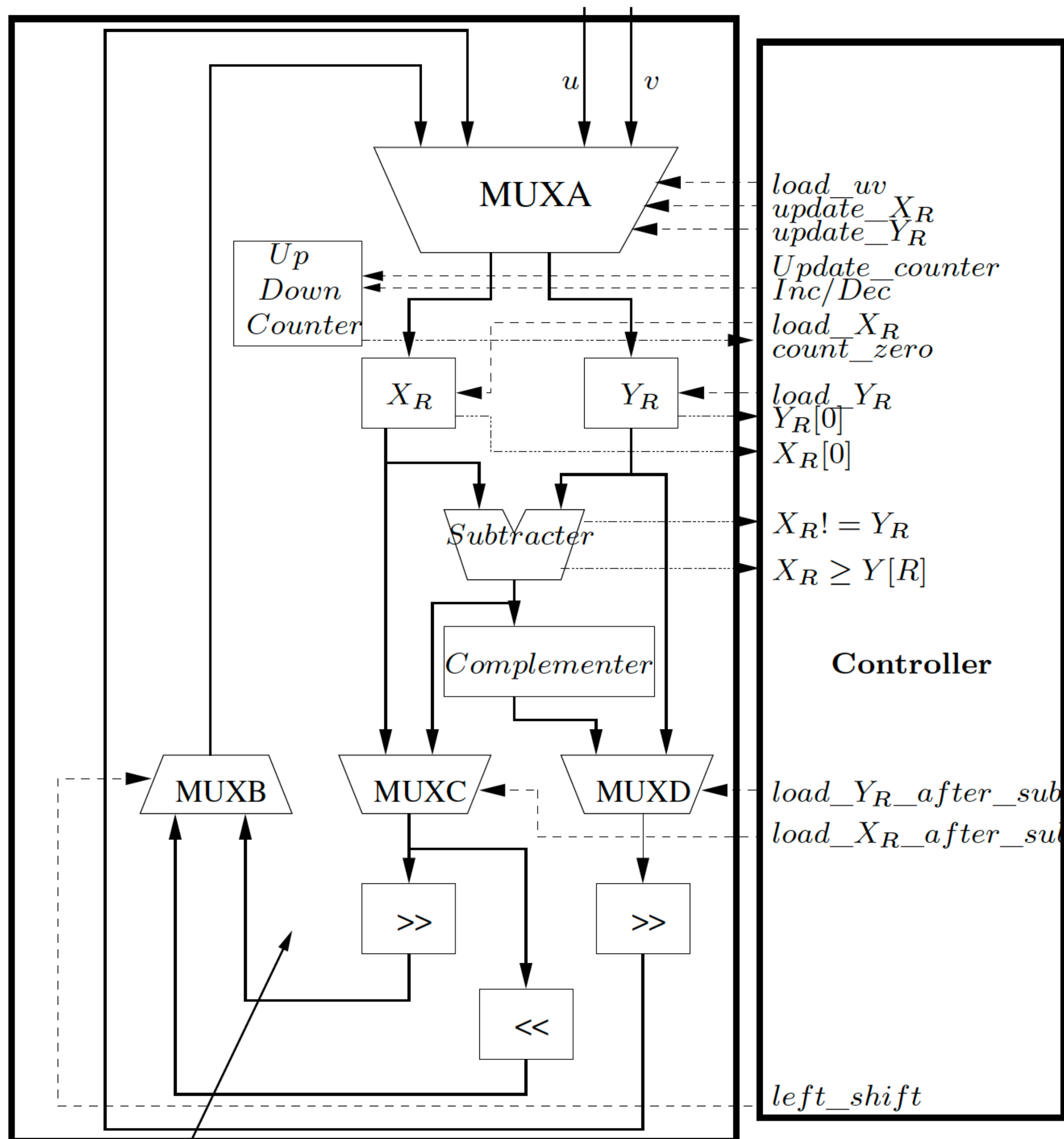

**Input:** Integers  $u$  and  $v$

**Output:** Greatest Common Divisor of  $u$  and  $v$ :  $z = \text{gcd}(u, v)$

```

1 register  $X_R, Y_R$ ;
2  $X_R = u; Y_R = v; \text{count} = 0$ ;
3 while ( $X_R \neq Y_R$ ) do
4   if ( $X_R[0] = 0$  and  $Y_R[0] = 0$ ) then
5      $X_R = \text{right shift}(X_R)$ 
6      $Y_R = \text{right shift}(Y_R)$ 
7      $\text{count} = \text{count} + 1$ 
8   end
9   else if ( $X_R[0] = 1$  and  $Y_R[0] = 1$ ) then
10     $Y_R = \text{right shift}(Y_R)$ 
11  end
12  else if ( $X_R[0] = 0$  and  $Y_R[0] = 1$ ) then
13     $X_R = \text{right shift}(X_R)$ 
14  end
15  else
16    if ( $X_R \geq Y_R$ ) then
17       $X_R = \text{right shift}(X_R - Y_R)$ 
18    end
19    else
20       $Y_R = \text{right shift}(Y_R - X_R)$ 
21    end
22  end
23 while ( $\text{count} > 0$ ) do
24    $X_R = \text{left shift}(X_R)$ 
25    $\text{count} = \text{count} - 1$ 
26 end
  
```

# Constructing the State Transition Table

Present State	Next State					Output Signals										
	0___	100__	110__	101__	111__	<i>load uv</i>	<i>update X<sub>R</sub></i>	<i>update Y<sub>R</sub></i>	<i>load X<sub>R</sub></i>	<i>load Y<sub>R</sub></i>	<i>load_X<sub>R</sub> after_sub</i>	<i>load_Y<sub>R</sub> after_sub</i>	<i>Update counter</i>	<i>Inc /Dec</i>	<i>left shift</i>	<i>count zero</i>
<i>S</i> <sub>0</sub>	<i>S</i> <sub>5</sub>	<i>S</i> <sub>1</sub>	<i>S</i> <sub>2</sub>	<i>S</i> <sub>3</sub>	<i>S</i> <sub>4</sub>	1	0	0	1	1	0	0	0	—	—	—
<i>S</i> <sub>1</sub>	<i>S</i> <sub>5</sub>	<i>S</i> <sub>1</sub>	<i>S</i> <sub>2</sub>	<i>S</i> <sub>3</sub>	<i>S</i> <sub>4</sub>	0	1	1	1	1	0	0	1	1	—	—
<i>S</i> <sub>2</sub>	<i>S</i> <sub>5</sub>	<i>S</i> <sub>1</sub>	<i>S</i> <sub>2</sub>	<i>S</i> <sub>3</sub>	<i>S</i> <sub>4</sub>	0	0	1	0	1	0	0	0	—	—	—
<i>S</i> <sub>3</sub>	<i>S</i> <sub>5</sub>	<i>S</i> <sub>1</sub>	<i>S</i> <sub>2</sub>	<i>S</i> <sub>3</sub>	<i>S</i> <sub>4</sub>	0	1	0	1	0	0	0	0	—	—	—
<i>S</i> <sub>4</sub> ( <i>X<sub>R</sub></i> ≥ <i>Y<sub>R</sub></i> )	<i>S</i> <sub>5</sub>	<i>S</i> <sub>1</sub>	<i>S</i> <sub>2</sub>	<i>S</i> <sub>3</sub>	<i>S</i> <sub>4</sub>	0	1	0	1	0	1	0	0	—	—	—
<i>S</i> <sub>4</sub> ( <i>X<sub>R</sub></i> < <i>Y<sub>R</sub></i> )	<i>S</i> <sub>5</sub>	<i>S</i> <sub>1</sub>	<i>S</i> <sub>2</sub>	<i>S</i> <sub>3</sub>	<i>S</i> <sub>4</sub>	0	0	1	0	1	0	1	0	—	—	—
<i>S</i> <sub>5</sub>	<i>S</i> <sub>5</sub>	<i>S</i> <sub>5</sub>	<i>S</i> <sub>5</sub>	<i>S</i> <sub>5</sub>	<i>S</i> <sub>5</sub>	0	0	0	0	0	0	0	1	0	1	0

- **Controller receives 4 input signals**
  - *X<sub>R</sub>* != *Y<sub>R</sub>*
  - *X<sub>R</sub>*[0]
  - *Y<sub>R</sub>*[0]
  - *X<sub>R</sub>* >= *Y<sub>R</sub>*

**Now go and code it down**